

SANT GADGE BABA AMRVATI UNIVERSITY, AMRAVATI
Summer Examination 2020 Credit Point
HVPM's College of Engineering and Technology, Amravati
Department of Electronics & Tele communication Engineering
Bachelor of Engineering Sem. :- VI

Subject :- LIC

Code :- 6XT2

Que1)

- a) **Explain the Internal block diagram of OP-AMP (2 credit)**
- b) Explain with circuit diagram the inverting & Non inverting OP AMP IC. (2 credit)
- c) Explain clipping & clamping circuit with waveform. (2 credit)
- d) Explain the block diagram of voltage regulator. (2 credit)
- e) Explain the block diagram of IC timer. (1 credit)
- f) Explain the block diagram of PLL. (1 credit)

Que 2)

- a) Explain the circuit diagram of 'constant current source' of OPAMP (2 credit)
- b) What is an Integrator, Explain with circuit diagram & wave forms. (2 credit)
- c) What is Schmitt trigger circuit Explain with circuit diagram & Wave forms. (2 credit)
- d) Explain the block diagram of IC723. (2 credit)
- e) Explain an Astable multivibrator using Timer IC 555 (1 credit)
- f) Draw & Explain the Transfer characteristics of PLL. (1 credit)

Que 3)

- a) What are the different frequency compensation methods of OPAMP. (2 credit)
- b) Draw & explain the circuit diagram of instrumentation amplifier. (2 credit)
- c) Draw & Explain the circuit diagram of 1st order High pass Butterworth filter using OPAMP. (2 cr)
- d) Draw the pin diagram of voltage regulator IC317. (2 credit)
- e) Explain monostable multivibrator using timer IC 555. (1 credit)
- f) Draw the pin diagram of function generator IC8038. (1 credit)

Que 4)

- a) Explain the Transfer characteristics of OPAMP. (2 credit)
- b) Explain with circuit diagram the differentiator circuit using OPAMP. (2 credit)
- c) Explain with diagram the 1st order Low Pass filter using OPAMP. (2 credit)
- d) What is short circuit protection in Voltage regulator. (2 credit)
- e) Explain the application of Timer IC as a FSK generator. (1 credit)
- f) Explain IC-565 PLL as AM detector. (1 credit)