

SANT GADGE BABA AMRVATI UNIVERSITY, AMRAVATI
Summer Examination 2020
HVPM's College of Engineering and Technology, Amravati
Department Of Computer Science & Engineering
Bachelor of Engineering Sem. :- III

Subject :-Electronics Devices & Circuits

Code :-3KS03/3KE03

Instructions:-

- 1) Solve any two questions
 - 2) All question carry equal marks
-

Q1.

- | | |
|---|----|
| a) Draw full bridge wave rectifier with capacitor filter. | 2M |
| b) Explain Early Effect? | 2M |
| c) What is bias compensation? | 1M |
| d) Give the comparison between BJT and JFET. | 2M |
| e) Draw BJT Wein Bridge oscillator | 2M |
| f) Explain working and application of LED. | 1M |

Q2.

- | | |
|--|----|
| a) What are the advantages of pi(π) filter | 2M |
| b) Explain how BJT can be used as a amplifier. | 2M |
| c) What is thermal runaway? | 1M |
| d) Draw the static characteristic of JFET. | 1M |
| e) Explain the operation of BJT Colpitts oscillator. | 2M |
| f) Explain the operation of LASER diode. | 2M |

Q3.

- | | |
|---|----|
| a) Give comparison of half wave and full wave rectifier | 2M |
| b) Derive the relationship between, I_{CBO} and I_{CEO} . | 1M |
| c) What is significance of DC load line? | 2M |
| d) Explain JFET parameter i) Drain resistance- ii) Trans conductance. | 2M |
| e) Draw working diagram of wein bridge oscillator. | 2M |
| f) What are Opto electronic Devices? | 1M |

Q4.

- | | |
|---|----|
| a) Explain operation of PN Junction diode. | 2M |
| b) How transistor acts as a amplifier. | 2M |
| c) What is need of biasing in transistor? | 1M |
| d) Draw the static characteristics of JFET. | 2M |
| e) Explain merits and demerits of crystal oscillator. | 1M |
| f) What Is Photovoltaic Effect? | 2M |