

SANT GADGE BABA AMARAVATI UNIVERSITY, AMARAVATI.
SUMMER EXAMINATION-2020
H.V.P.M.'s College of Engineering and Technology, Amravati.
Department of Electronics and Telecommunication
Bachelor of Engineering Semester IV.


Subject : Digital Electronics – I

Subject code : 4ET4

Instructions:-

 - i) Solve any two questions.
- ii) All questions carry equal marks.


- Que 1**
- a) Explain in brief Transistor-Transistor logic (TTL) circuit with active pull up arrangements. Verify the logic operations given by TTL 2 credit pts
 - b) Minimize the following logic function and realize using NAND gates only. $f_1(A, B, C, D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$ 2 credit pts
 - c) Implement the following logical expression using 8:1 MUX $F = \sum m(0,1, 2,3,4,10,11,14,15)$ 2 credit pts
 - d) What is Race around condition? How it is overcome? Explain master-slave J-K flip flop with proper table 2 credit pts
 - e) Obtain reduced state table and reduced state diagram for the sequential machine whose state diagram is shown below 1 credit pts



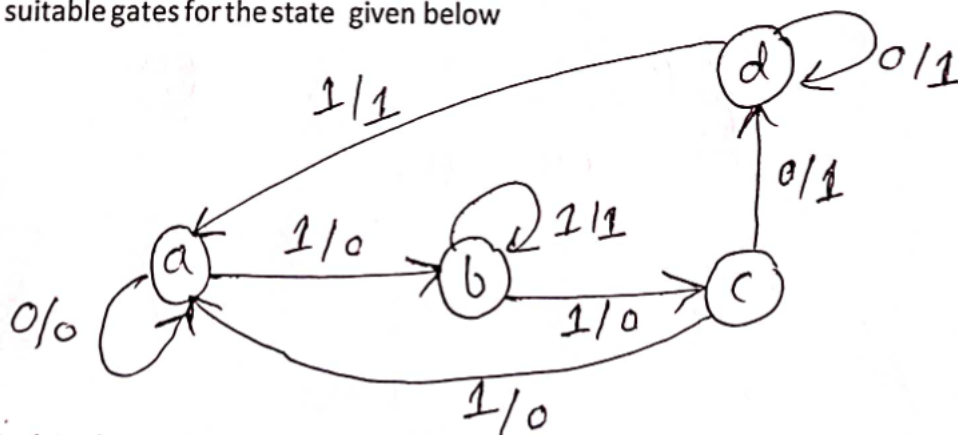- f) Explain in brief (i) PROM (ii) EEPROM (iii) EPROM 1 credit pts

- Que 2**
- a) Perform the following using 2's complement method
 (1) $(48)_{10} - (23)_{10}$ 2 credit pts
 (2) $(48)_{10} - (-23)_{10}$
 (3) $(-48)_{10} - (23)_{10}$
- b) Design the combinational circuit for full adder and implement it using suitable gates. 2 credit pts
- c) Design 5-line to 32-line decoder circuit using 4-line to 16-line decoders and suitable gate. 2 credit pts
- d) Design 4-bit parallel in serial out right shift register using D-Flip Flops and suitable gates. 2 credit pts
- e) The state diagram and state table for a Moore type sequence detector to detect the sequence 1110. 1 credit pts
- f) Explain the working of dynamic RAM cell. 1 credit pts

- Que 3**
- a) 1) Perform the following: 2 credit pts
 (i) $(BC5)_{16} - (A2B)_{16} = (?)_2$, (ii) $(287)_{10} = (?)_{\text{gray}}$
 (iii) $(0.65625)_{10} = (?)_2$ (iv) $(327.89)_{10} = (?)_{\text{BCD}}$
- b) Design and explain one digit BCD adder circuit using 4-bit adder IC 74LS83 and required gates. Explain with the help of suitable example. 2 credit pts
- c) Design 5-bit comparator using single 7485 IC and suitable gate. Also explain its operation. 2 credit pts
- d) State differences between synchronous and asynchronous counters. 2 credit pts
- e) Design a clocked sequential circuit using T-Flip Flops and suitable gates for the state given below. 1 credit pts



- f) Explain the read cycle timing parameters of a memory using proper timing diagram. 1 credit pts

Que 4

- a) Explain TTL with active pull up. Give its significance. 2 credit pts
- b) Design binary to gray code converter circuit using suitable gate . 2 credit pts
- c) The truth table for an ROM to implement the given function :
 $f = \sum m(1,2,4,6)$ 2 credit pts
- d) Design a synchronous counter to count the sequence 1-2-5-3-0-7 using T- F-F. 2 credit pts
- e) Define an asynchronous sequential circuits . How its differs from synchronous sequential circuits. 1 credit pts
- f) With neat circuit diagram explain the operation of bipolar static RAM Cell 1 credit pts

