

**Sant Gadge Baba Amravati University, Amravati Summer 2020 Exam**

**H.V.P.Mandal's College of Engineering & Technology Amravati**

**Course: Computer Science & Engineering**

**BE Four Year Fifth Semester (Computer Science & Engineering) Summer 2020 Exam  
5KS04 Switching Theory and Logic Design**

**ONLY FOR BACKLOG STUDENTS**

---

**Note:**

- 1. Solve any Two Questions.**
- 2. Each Question carries 10 marks.**

**Question No.1 (10 marks)**

a. Explain the scalar type in VHDL.	<b>2M</b>
b. Write a VHDL code for AND gate using behavioral style of modeling.	<b>2M</b>
c. What is Quine-McClusky method?	<b>1M</b>
d. Which logic device is called as a distributor? 1) Multiplexer 2) demultiplexer 3) encoder 4) decoder	<b>1M</b>
e. What are the applications of flip-flops?	<b>2M</b>
f. Compare the Moore and Mealy machines.	<b>2M</b>

**Question No.2 (10 marks)**

a. What is Identifiers in VHDL? Explain.	<b>2M</b>
b. How to declare entity in VHDL?	<b>2M</b>
c. What is a standard SOP form?	<b>1M</b>
d. What is a parallel adder?	<b>2M</b>
e. Explain the operation of JK flip-flop.	<b>2M</b>
f. What is the Moore machine?	<b>1M</b>

**Question No.3 (10 marks)**

a. Explain how data will be manipulated using sequential statements with one example.	<b>2M</b>
b. Write short note on architectural bodies.	<b>2M</b>
c. What is k-map? What are its advantages and disadvantages?	<b>2M</b>
d. Distinguish between parallel adder and serial adder.	<b>2M</b>
e. List the different types of latches and flip-flops.	<b>1M</b>

f. What do you mean by terminal state?

**1M**

**Question No.4 (10 marks)**

a. Explain the standard logic (std\_logic) in VHDL.

**1M**

b. Explain entity instantiation and port mapping in VHDL.

**1M**

c. Reduce the following expression using k-map.

$$\sum m(5,6,7,9,10,11,13,14,15)$$

**2M**

d. With the help of a logic diagram explain a parallel adder/subtractor using 2's complement system.

**2M**

e. Distinguish between combinational and sequential sequence switching circuits.

**2M**

f. What are the capabilities and limitations of finite state machines?

**2M**